

CURRENT ELECTRICITY

→ Electric Current:- The rate of directional flow of electric charge.

- Scalar quantity
- Moves in the direction of motion of +ve charge
- Unit (Ampere → A), dimension $[A^1]$


Electric current

$$I_{\text{inst}} = \frac{dq}{dt}$$

slope of q/t graph


$$I_{\text{avg}} = \frac{\Delta q}{\Delta t} = \frac{q_f - q_i}{\Delta t}$$
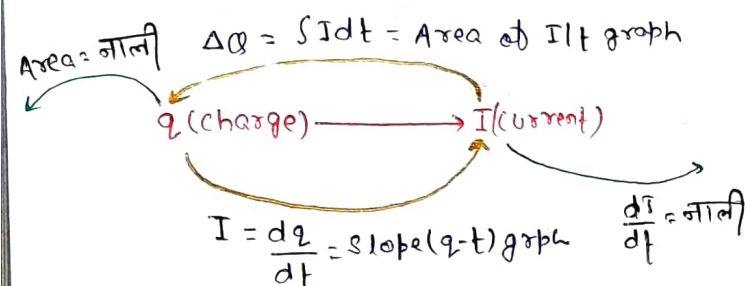
$$I_{\text{avg}} = \frac{\int Idt}{\int dt}$$



Q → Ratio of current through wire A to B
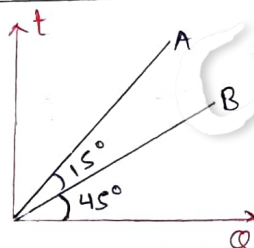
$$\frac{I_A}{I_B} = \frac{\tan 30^\circ}{\tan 45^\circ} = \frac{1}{\sqrt{3}}$$



Q → If 'n' electron moving on circular path with frequency 'f', find current?

$$I = nef$$


Isolated conductor

- Not connected to the battery.
- large no. of e^- are in random motion.

$$ne^- = 10^{28} e^- / m^3$$

n = no. of free e^- per

unit volume
Unit = m^{-3}

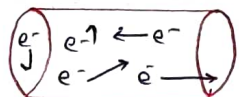

$$E_{\text{in}} = 0, V = 10^3 - 10^4 \text{ V/m}$$

$$V_{\text{avg}} = 0$$

$$\text{Speed} \propto \sqrt{\text{Temp}}$$

$$\text{Temp} \uparrow \rightarrow \tau \downarrow$$

τ (relaxation time)

↳ Avg. time b/w two collision

$$\frac{1}{2} mv^2 = \frac{3}{2} k_B T$$

$$k_B = 1.38 \times 10^{-23} \frac{J}{K}$$

Battery connected to conductor


$$F_e = qE = eE, E = \frac{V}{l}$$

$$a = \frac{qE}{m_e} = \frac{eE}{m_e} \text{ (uniform)}$$

$$v_D = v + at$$

$$v_D = \frac{eE\tau}{m}$$

$$I = neAv_D$$

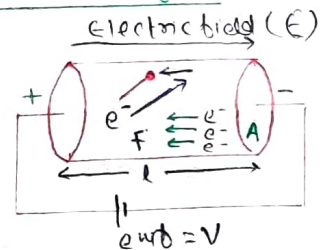

Ohm's law: - $V = IR$

Resistivity / Resistance / Conductance

$$\sigma = \frac{ne^2\tau}{m}$$

$$\text{Resistivity} \rightarrow \rho = \frac{1}{\sigma} \rightarrow \text{Conductance}$$

$$\rho = \frac{m}{ne^2\tau}$$

$$R = \frac{\rho l}{A}$$

Material properties

MR* feel

$$\sigma = \frac{ne^2\tau}{m} \rightarrow \rho = \frac{1}{\sigma} \rightarrow \rho = \frac{m}{ne^2\tau}$$

$$R = \frac{\rho l}{A}$$

$$V = \frac{mI}{ne^2\tau A}$$


Microscopic form of Ohm's law

$$R = \frac{mI}{ne^2\tau A} \rightarrow V = IR \rightarrow \text{Macroscopic form of Ohm's law}$$

Mobility:- property of charge particle.

- does not depend on drift velocity & Electric field.
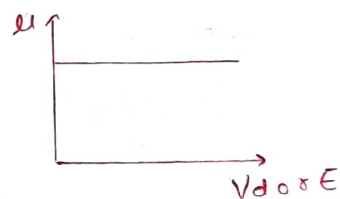
$$\mu = \frac{v_D}{E} = \frac{e\tau}{m}$$



$$\mu_e > \mu_p > \mu_D = \mu_A$$

Current density: - (J)

- vector, unit $\rightarrow \text{Amp}/m^2$
- direction along current.

$$J = \frac{I}{A}$$

$$I = \vec{J} \cdot \vec{A} = JA \cos \theta$$

$$\vec{J} = ne\vec{v}_D$$


$$\vec{J} = \sigma \vec{E}$$

Vector form of Ohm's law

Current:- $I_A = I_B$

current density:- $J_A < J_B$

Drift velocity:- $v_A < v_B$

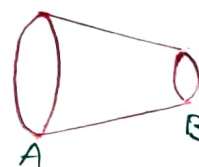

★ NOTE

If Temp ↑

Conductor

$\sigma \downarrow$ $\rho \uparrow$

$V_d \downarrow$ $\tau \downarrow$

Randomness ↑

Insulator

Same as semi-conductor but in small amount

Semi-conductor

e^- hole pair ↑
 $\sigma \uparrow$
 $\rho \downarrow$

Resistance

$$R \propto l \propto \frac{1}{A}$$

$$R = \frac{\rho l}{A}$$

① If Area (A) = constant

$$R \propto l$$

$$\frac{R_1}{R_2} = \frac{l_1}{l_2}$$

$$\left[100 \times \frac{\Delta R}{R} \right] = \left[\frac{\Delta l}{l} \times 100 \right] \rightarrow \text{for small change}$$

② If Length (L) = constant

$$R \propto \frac{1}{A}$$

$$\frac{R_1}{R_2} = \frac{A_2}{A_1} = \left(\frac{r_2^2}{r_1^2} \right)$$

$$\frac{\Delta R}{R} = -\frac{\Delta A}{A}$$

$$\frac{\Delta R}{R} = -\frac{2\Delta r}{r}$$

③ If Volume (V) = constant (stretched)

$$R = \frac{\rho l}{A} \times \frac{1}{l}$$

$$R = \frac{\rho l^2}{V}$$

$$R \propto l^2$$

$$\frac{R_1}{R_2} = \left(\frac{l_1}{l_2} \right)^2$$

$$\frac{\Delta R}{R} = \frac{2\Delta l}{l}$$

$$R = \frac{\rho (l \times A)}{A \times A} = \frac{\rho V}{A^2}$$

$$R \propto \frac{1}{A^2} \propto \frac{1}{r^4}$$

$$\frac{\Delta R}{R} = -\frac{2\Delta A}{A} = -\frac{4\Delta r}{r}$$

$$\frac{R_1}{R_2} = \left(\frac{A_2}{A_1} \right)^2 = \left(\frac{r_2}{r_1} \right)^4$$

Temp^o coefficient of linear expansion

$$\alpha = \frac{\Delta l}{l \Delta T}$$

Temp^o coefficient of Areal expansion

$$\beta = \frac{\Delta A}{A \Delta T}$$

Relation b/w temp^o coefficient of

(a) Linear expansion

(b) Areal expansion

$$\beta = 2\alpha$$

Temp^o coefficient of Resistance

$$\alpha_R = \frac{\Delta R}{R_0 T}$$

R_T = Resistance at temp^o T

R_0 = Resist. at 0°C

$$R_T = R_0 (1 + \alpha T)$$

Temp^o coefficient of Resistivity

$$\alpha_\rho = \frac{\Delta \rho}{\rho_0 \Delta T}$$

Relation b/w temp^o coefficient of:-

(a) linear expansion (α)

$$R = \frac{\rho l}{A}$$

(b) Resistance (α_R)


(c) Resistivity (α_ρ)

$$\alpha_R = \alpha_\rho + \alpha$$

Cell (Battery)

Terminal potential in discharging of Battery:-

$$V_T = (V_A - V_B) = E - I\tau$$

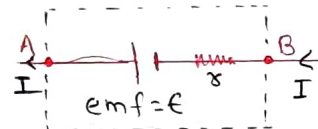

Ideal Battery :- ($\tau = 0$)

$$V_T = E - I \times 0$$

$$V_T = E$$


Not connected in circuit:-

$$V_T = E - I\tau = E - 0 \times \tau$$

$$V_T = E$$


Charging of Battery:-

$$V_T = E + I\tau$$

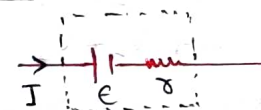

Discharging of Battery

$$V_T = E - I\tau$$

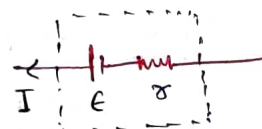

Combination of Resistance

① In series :- $[I = \text{same}]$, $[V = \text{diff}]$

$$V_{\text{total}} = V_1 + V_2 + V_3 + \dots$$

$$R_{\text{eq}} = R_1 + R_2 + R_3 + \dots$$

⇒ If n equal resistance

$$R_{\text{eq}} = nR$$

⇒ $V \propto R \rightarrow$ Jitna jyada 'R' utna jyada V_{drop} .

② In parallel :- $[V = \text{same}]$, $[I = \text{diff}]$

$$I_{\text{total}} = I_1 + I_2 + I_3 + \dots$$

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

⇒ If n equal resistance


$$R_{\text{eq}} = \frac{R}{n}$$

↳ Household circuit = Parallel circuit

⇒ $I \propto \frac{1}{R} \rightarrow$ Jitna kam 'R' utna jyada 'I'.


Potential at Mid-Point
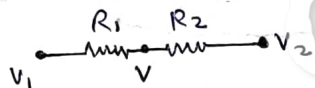
$$V_{\text{mid}} = \frac{\frac{V_1}{R_1} + \frac{V_2}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}}$$



Combination of cell

① Series combination of cell

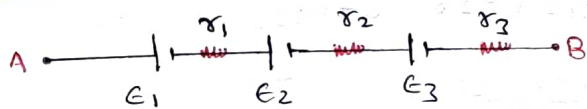


$$E_{\text{net}} = E_1 + E_2 + E_3$$

$$r_{\text{net}} = r_1 + r_2 + r_3$$

⇒ If there are n identical battery is connected in series.

$$E_{\text{net}} = nE, \quad r_{\text{net}} = nr$$

② Parallel combination of cell

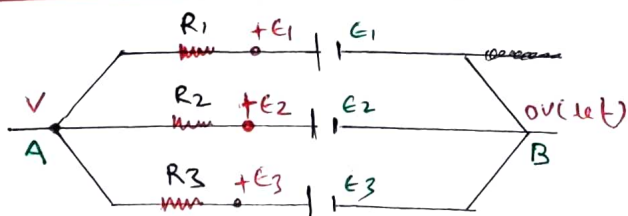

$$E_{\text{eq}} = \frac{E_1}{R_1} + \frac{E_2}{R_2} + \frac{E_3}{R_3}$$

$$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{r_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$V_{AB} = (V - 0) = \frac{E_1}{R_1} + \frac{E_2}{R_2} + \frac{E_3}{R_3}$$

$$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

⇒ If there are n identical cell in parallel


$$E_{\text{net}} = E (\text{ewb}), \quad r_{\text{eq}} = r/n$$

③ Mixed combination of cell

↳ n -identical battery (E, r) connected in series, then this series combination connected m -times parallel with external resistance R .


$$I = \frac{n m E}{m r + R}$$

#

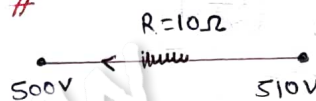

$$I = \frac{510 - 500}{10}$$

$$I = 1A$$

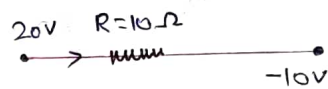


$$I = \frac{20 - (-10)}{10} = 3A$$

⇒ Find potential drop across R_1 and R_2

$$I = \frac{V}{R_1 + R_2}$$


$$V_1 = I R_1 = \frac{V R_1}{R_1 + R_2}$$

$$V_2 = \frac{V R_2}{R_1 + R_2}$$

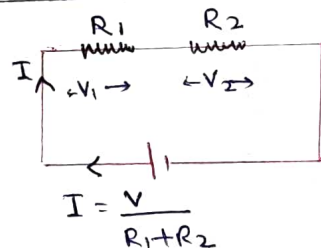


⇒ Find potential at junction
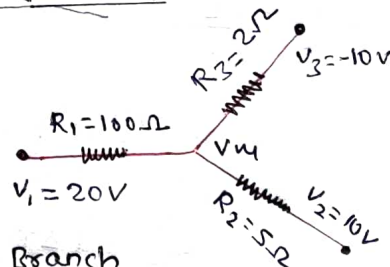
$$V_{\text{M}} = \frac{\frac{20}{10} + \frac{10}{5} - \frac{10}{2}}{\frac{1}{10} + \frac{1}{5} + \frac{1}{2}}$$



⇒ Find current in BD Branch
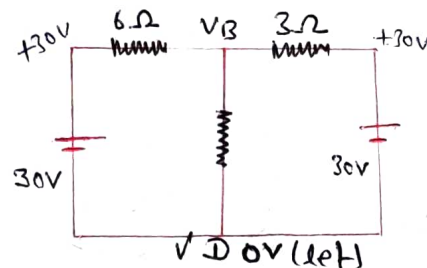
$$V = \frac{\frac{30}{6} + \frac{0}{3} + \frac{30}{3}}{\frac{1}{3} + \frac{1}{6} + \frac{1}{3}}$$




Wheat stone bridge

$$V_x = V_y$$

Current in $R_5 = 0$

$$\frac{R_1}{R_3} = \frac{R_2}{R_4}$$

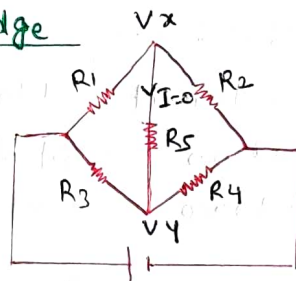

Power

• Scalar, unit $\rightarrow$ watt (W)

$$E = Pt$$

$$I^2 R t = Pt$$

$$P = I^2 R = \frac{V^2}{R} = IV$$

Joules law of Heating effect / Power loss

$$\begin{aligned} \text{Heat (H)} &\propto I^2 \\ &\propto R \\ &\propto t \end{aligned}$$

$$H = I^2 R t = \left(\frac{V^2}{R} \right) t = V I t$$



$$H = m \Delta \theta S \propto$$

Maximum Power theorem


$$P = \frac{\epsilon^2}{(R+r)^2} R$$

Power drop will be maximum when $(r=R)$


$$P_{\max} = \frac{\epsilon^2}{4R}$$

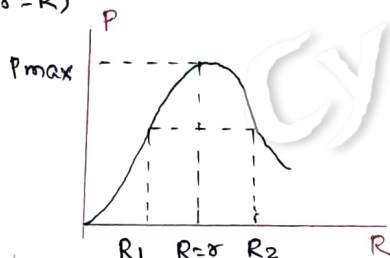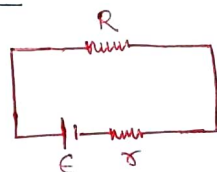

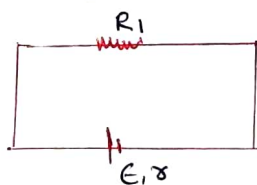$\Rightarrow$ If Power drop is same in both R_1 & R_2 then find R b/w R_1 , R_2 and r .



$$I_1 = \frac{E}{R_1 + r}$$

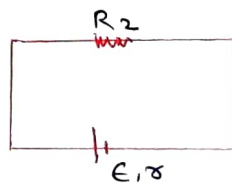

$$I_2 = \frac{E}{R_2 + r}$$

$$\frac{\sqrt{R_1}}{R_1 + r} = \frac{\sqrt{R_2}}{R_2 + r} \Rightarrow r = \sqrt{R_1 R_2}$$

Time taken to boil same amount of water when connected in

(a) Series

$$t = t_1 + t_2$$

(b) Parallel

$$\frac{1}{T} = \frac{1}{t_1} + \frac{1}{t_2}$$

Bulb :- (Pure resistance hai)


$$R_{\text{bulb}} = \frac{V_R^2}{P_R}$$

$$P_{\text{cons.}} = \left[\frac{V_S}{V_R} \right]^2 P_{\text{rated}}$$

$$R_{\text{bulb}} \propto \frac{1}{P_{\text{rated}}}$$

① Series combination
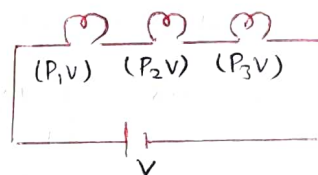
$$\frac{1}{P_{\text{cons.}}} = \frac{1}{P_1} + \frac{1}{P_2} + \frac{1}{P_3}$$



If all are identical bulb

$$P_{\text{cons.}} = \frac{P}{n}$$

$$\text{Brightness} \propto P_{\text{cons.}} \propto R_{\text{bulb}} \propto \frac{1}{P_{\text{rated}}}$$

$$P_{\text{cons.}} = i^2 R_{\text{bulb}}$$

#

B ₁	B ₂	B ₃
50W	100W	250W
220V	220V	220V


Brightness
($B_3 > B_1 > B_2$)

② Parallel combination

$$P_{\text{cons.}} = P_1 + P_2 + P_3$$

If all are identical bulb

$$P_{\text{cons.}} = nP$$

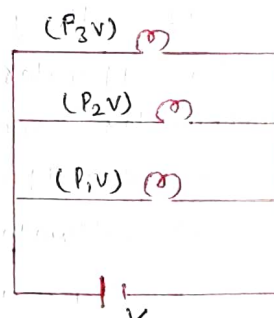

$$\text{Brightness} \propto P_{\text{cons.}} \propto \frac{1}{R_{\text{bulb}}} \propto P_{\text{rated}}$$

$$P_{\text{consumed}} = \frac{V^2}{R_{\text{bulb}}}$$

#

Brightness

($B_2 > B_3 < B_1$)

B ₁	(50W, 220V)
B ₂	(150W, 220V)
B ₃	(100W, 220V)

220V


Galvanometer

- An instrument use to detect or measure small current
- Very sensitive, produce large error
- I_G = Max^m current that can blow
- G = resistance of galvanometer.

⇒ As Ammeter :- (measure current)

- Shunt (small) connect in parallel with galvanometer.
- Ammeter connected in series with circuit to measure current.
- Ideal $R=0$; Behave as simple wire
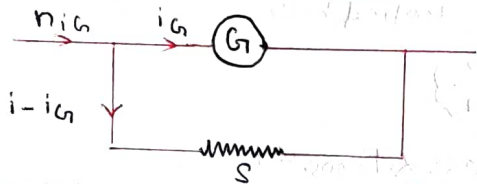
$$\% \text{ Error} = \frac{i_T - i_M}{i_T} \times 100$$



$$R_{\text{ammeter}} = \frac{GS}{G+S}$$

$$S = \frac{G}{n-1}$$

$n = \frac{(I) \text{ we want to measure}}{(I) \text{ jitha galvanometer se Jayega}}$

⇒ As Voltmeter :- (measure voltage)

- Shunt (large) resistance connected in series with galvanometer to convert into voltmeter
- voltmeter connected in parallel to measure voltage.
- Ideal voltmeter ($R = \text{Infinite}$)
↳ Behave as open wire


$$\% \text{ Error} = \frac{V_T - V_M}{V_T} \times 100$$

$$R_{\text{voltmeter}} = G + S$$

$$S = G(n-1)$$

Meter Bridge

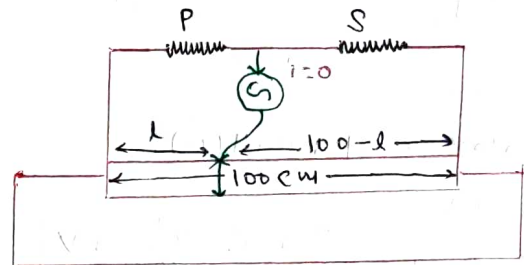- An instrument used to measure resistance
- Based on concept of wheat stone bridge.
- Resistance per unit length $\lambda = \left(\frac{R}{L}\right)$



$$\frac{P}{Q} = \frac{l}{100-l}$$